



# Introduction to Path Delay Fault And A Sat-Based Path-Delay-Fault ATPG Solver


VLSI Testing LAB: ED612

陳玓融 rosechen30932@gmail.com

陳柏諺 chentt13@gmail.com
 
# Path Delay Fault

- Any path with a total delay exceeding the clock interval is called a "path fault."
- One major problem in finding delay faults is the number of possible paths in a circuit under test (CUT). The number of total paths can grow exponentially with circuit size.




4 paths in the circuit:

- $A \rightarrow E \rightarrow G$
- $B \rightarrow E \rightarrow G$
- $C \rightarrow F \rightarrow G$
- $D \rightarrow F \rightarrow G$
 
# Path-Delay-Fault ATPG


- A path-delay-fault ATPG generates a vector pair  $(v1, v2)$  that can distinguish between the correct circuit behavior and the faulty circuit behavior caused by defects.
- 2 phases of ATPG:
  - **Fault Activation**: Creates a transition (either rising or falling) at the beginning of the target path.
  - **Fault Propagation**: Propagates the corresponding transition to primary output through the target path.

Output of ATPG:  
 $(v1, v2)$   
Ex. 0111 , 1111



# Some Terms in Path-Delay-Fault ATPG

## □ On-input & off-input

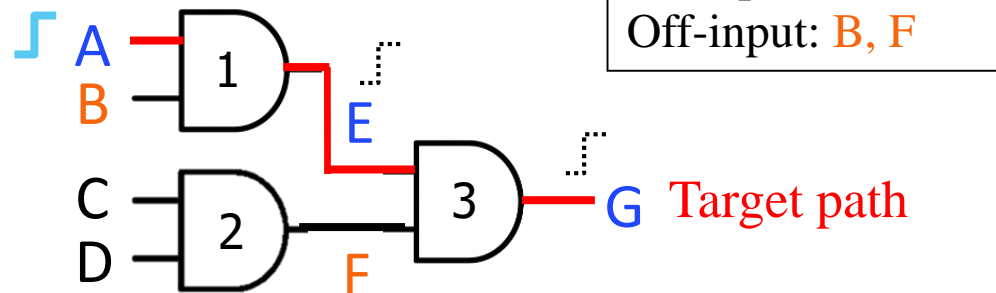

## □ Controlling Values & Non-Controlling Values

Gate Type	Controlling Value (CV)	Non-Controlling Value (NCV)
AND	0	1
OR	1	0

## □ Timeframe


Transition Type	Logic value at Timeframe 0	Logic value at Timeframe 1
Rising(0→1)	0	1
Falling(1→0)	1	0

# Test Quality for A Path

- A test pattern (v1,v2) of a path P can be classified as Robust or Non-Robust based on the transition states on the on-inputs and off-inputs.


Output of ATPG:  
(v1, v2)

R: 1111 , 0111  
NR: 1XXX , 0111

 


On-input transition	Off-input assignments	
	Robust(R)	Non-Robust(NR)
cv $\rightarrow$ ncv	x $\rightarrow$ ncv	x $\rightarrow$ ncv
ncv $\rightarrow$ cv	ncv $\rightarrow$ ncv	x $\rightarrow$ ncv


# Robust Test

 


	$t_0$	$t_1$
A	0	1
B	0	1
C	0	1

 

 - ☐ Both inputs have delay fault
  - Success




 - ☐ Only on-input has delay fault
  - Success




- ☐ Only off-input has delay fault
  - Success


# Non-Robust Test

 


	$t_0$	$t_1$
A	1	0
B	0	1
C	0	0

 

 - ☐ Both inputs have delay fault
  - Fail



 - ☐ Only on-input has delay fault
  - Success



- ☐ Only off-input has delay fault
  - Fail

# Boolean Satisfiability (SAT) Problem

---

- SAT is the problem of determining if there exists an interpretation that satisfies a given Boolean formula.
  - $(\neg a \wedge b)$  is satisfiable because  $a=0$  and  $b=1$  make it true.
  - $(\neg a \wedge a)$  is unsatisfiable.
- SAT is the first problem that was proven to be NP-complete which means there is no known algorithm that efficiently solves each SAT problem.
- A 3-CNF-SAT problem: Given a Boolean formula  $\mathbb{F}$  in 3-CNF form, does there exist any interpretation that make  $\mathbb{F}$  true?






# Conjunctive Normal Form (CNF)

- A literal is either a Boolean variable or the negation of a Boolean variable.
  - $x, \neg y$
- A clause is a disjunction of literals.
  - $(x \vee y \vee \neg z)$
- A Boolean formula is in Conjunctive Normal Form if it is a conjunction of clauses (or a single clause).
  - $(x \vee y \vee \neg z \vee w \vee \neg u) \wedge (\neg y \vee z) \wedge (\neg x)$
  - $(x \vee y \vee \neg z \vee w \vee \neg u)$
- 3-CNF: a conjunction of clauses where each clause contains exactly 3 literals/at most 3 literals.
  - $(x \vee y \vee \neg z) \wedge (\neg y \vee z) \wedge (\neg x)$


# Tseytin Transformation

- Tseytin transformation takes as input an arbitrary combinatorial logic circuit and produces a Boolean formula in conjunctive normal form (CNF), which can be solved by a CNF-SAT solver.

Gate type	Operation	CNF expressions
	$c = a \cdot b$	$(\neg a \vee \neg b \vee c) \wedge (a \vee \neg c) \wedge (b \vee \neg c)$
	$c = a + b$	$(a \vee b \vee \neg c) \wedge (\neg a \vee c) \wedge (\neg b \vee c)$
	$c = \neg a$	$(\neg a \vee \neg c) \wedge (a \vee c)$
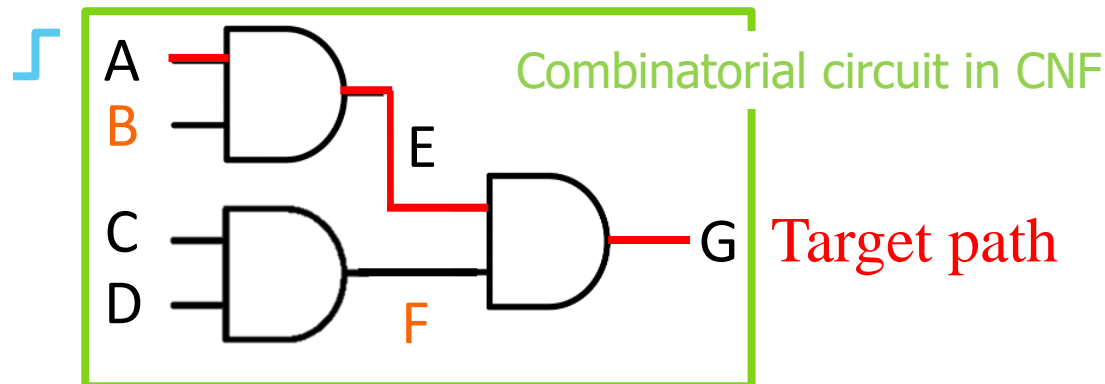
# SAT-Based Path-Delay-Fault ATPG

- A given combination circuit + a given PDF.
- Do **Fault Activation** & **Fault Propagation** = Build a Boolean formula in CNF and feed into the SAT solver.
  - Problem definition: Can we find a test vector pair to detect the transition delay fault rising on path  $A \rightarrow E \rightarrow G$  ?



For non-robust test:

1<sup>st</sup> timeframe:  $(\neg A \vee \neg B \vee E) \wedge (A \vee \neg E) \wedge (B \vee \neg E) \wedge \dots \wedge \neg A$

2<sup>nd</sup> timeframe:  $(\neg A \vee \neg B \vee E) \wedge (A \vee \neg E) \wedge (B \vee \neg E) \wedge \dots \wedge A \wedge B \wedge F$

- If the SAT problem is solved, a test vector pair(v1, v2) is successively found and the PDF is detected.

# What you need to do in HW4 In kai\_objective.cpp

- Add more clauses to the original combinational circuit CNF by using `AddObj(ToCUTName(gate ptr, timeframe), logic value)`

`void AtpgObj::BuildFromPath_NR(PATH 0 or 1 *pptr) 0 or 1 Target path`

```
{
    cleanup();
    KaiGATE *CurG, *PreG;
    TRANSITION CurT, PreT;
    assert(pptr->NoGate() == pptr->NoTrans());
```

```
PreG=/* input gate on sensitive path*/
PreT=/* input transition on sensitive path*/
```

Find PI gate ptr and the transition state of the PI on target path

```
// Fault Activation at 1st TimeFrame
if(PreT==R) AddObj(ToCUTName(PreG, 0), /*value*/);
else if(PreT==F) AddObj(ToCUTName(PreG, 0), /*value*/);
else { cerr<<"R/F Error !"<<endl; exit(-1); }

// Fault Activation at 2nd TimeFrame
if(PreT==R) AddObj(ToCUTName(PreG, 1), /*value*/);
else if(PreT==F) AddObj(ToCUTName(PreG, 1), /*value*/);
else { cerr<<"R/F Error !"<<endl; exit(-1); }
```

Fault Activation

```
/*Fault Propagation = off-input setting on sensitive path */
```

Fault Propagation

# More Hints

- Go to the following files to understand the data structure of this program.

```
#include "GetLongOpt.h"
#include "kai_gate.h"
#include "kai_path.h"
#include "kai_objective.h"
#include "kai_typeemu.h"
```

- E.g. In kai\_path.h:

```
KaiGATE* GetGate(unsigned int i) { return _vgate[i]; }
TRANSITION GetTrans(unsigned int i) { return _vtrans[i]; }
unsigned int NoGate() { return _vgate.size(); }
```

- E.g. In kai\_gate.h:

```
GATEFUNC GetFunction() { return _function; }
KaiGATE* Fanin(unsigned int i) { return _fanin[i]; }
```

- Only AND, NAND, OR, NOR gates need to be considered.